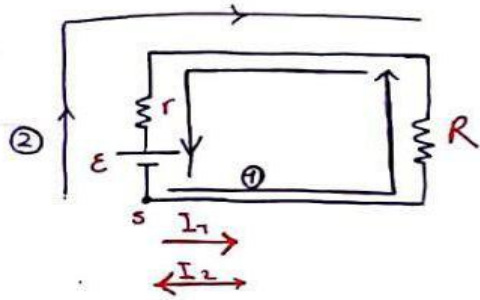



کانال یازدهم ریاضی

قاعده حلقه :



$$\begin{cases} \text{جهت حرکت} \\ \text{①} \end{cases} \begin{cases} -I_1 R - I_1 r - \varepsilon = 0 \\ +I_2 R + I_2 r - \varepsilon = 0 \end{cases}$$
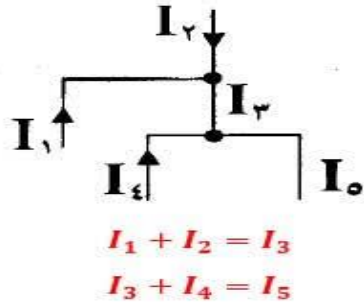
$$\begin{cases} \text{جهت حرکت} \\ \text{②} \end{cases} \begin{cases} +\varepsilon + I_1 r + I_1 R = 0 \\ +\varepsilon - I_2 r - I_2 R = 0 \end{cases}$$




$$\begin{aligned} I_1 + I_2 &= I_3 \\ I_3 + I_4 &= I_5 \end{aligned}$$

حانه نجابی

تربیب مقادیرها


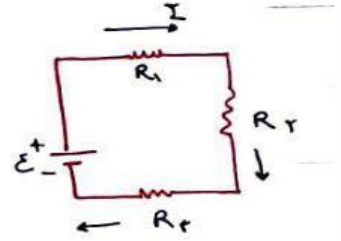
$$I = \frac{\varepsilon}{R_1 + R_r + R_r}$$



$$R_{eq} = R_1 + R_r + R_r$$

$$V = \varepsilon = V_1 + V_r + V_r$$
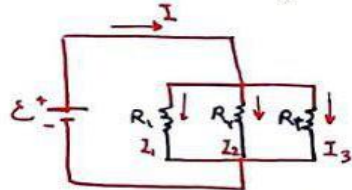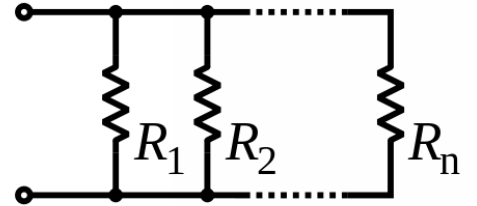
$$R_{eq} = R_1 + R_r + R_r + \dots + R_n$$



$$I = I_1 + I_2 + I_3$$

$$V_1 = V_2 = V_3 = V$$

$$I_1 = \frac{V}{R_1}$$

$$I_2 = \frac{V}{R_2}$$

$$I_3 = \frac{V}{R_3}$$

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots + \frac{1}{R_n}$$

